 




SINCLAIR QL CSYNC-INVERTER

The QL cannot be connected to a CGA monitor directly. This is because the QL has an active-low Csync pin. A CGA monitor expects an active-high signal. This document shows how to make a very little circuit board, which inverts the Csync pin. No additional power supply is needed. The PCB is small enough to fit inside a DB-9 connector.



Here are some pictures of the cable.


The circuit is straightforward. The Csync signal is fed through a single gate NAND, which acts as the inverter. The NAND gate is powered by the Csync signal itself. Energy is stored in a 10uF tantalum capacitor, to buffer the time the Csync signal is low. A 100 ohm resistor is added to limit the inrush current during power-up. Some additional resistors and SOT-23 transient suppressors are added for extra protection of the QL.

  

Here you can see the 'original' Csync signal, measured directly at the 8-pin DIN connector at the rear of the QL.


Inverted signal

QL monitor pinout

 

| | | |
|---|-------|----------------------|
| 1 | PAL | Composite PAL |
| 2 | GND | Ground |
| 3 | Video | Composite Mono Video |
| 4 | Csync | Composite Sync |
| 5 | Vsync | Vertical Sync |
| 6 | Green | Color Signal |
| 7 | Red | Color Signal |
| 8 | Blue | Color Signal |

CGA DB-9 pinout

 

| | | |
|---|-------|---------------------|
| 1 | GND | Ground |
| 2 | GND | Ground |
| 3 | Red | Color Signal |
| 4 | Green | Color Signal |
| 5 | Blue | Color Signal |
| 6 | - | |
| 7 | - | |
| 8 | Hsync | (Inverter QL-Csync) |
| 9 | Vsync | Vertical sync |

The schematic drawing is shown on the following page.
The following components are needed:

| Qty | RefDes | Component | Value | Description | PatternName |
|-----|----------|-------------|-------|-----------------|-------------|
| 1 | U1 | 74AHC1G00GW | | SingleGate NAND | SOT353 |
| 1 | R2 | ARC241 | 100R | Resistor Array | ARC241 |
| 1 | D1 | BAV70W | | Dual Diode | SOT323 |
| 1 | C1 | CAP_SIZEA | 10uF | Tantalum Cap. | SIZE_A |
| 1 | K3 | DB9M_EDGE | | SubD Connector | DB9EDGEM |
| 3 | Z1,Z2,Z3 | MMBZ6V2ALT1 | 6.2V | Transient Abs. | SOT23 |
| 2 | R1,R3 | RES_0603 | 100R | Resistor | 0603 |

Additional stuff:

6 core cable (screened if possible).

8 pin QL style DIN connector.

Sub-D hood. ADT09 from Assmann, www.assmann.com, see picture on first page.

2 Washers, which are below the two screws inside the sub-D hood. See picture.

The circuitboard itself.

Mail me if you need any gerberfiles or additional info.

Don't fry your QL building this circuit! Good luck!

Marcel Flipse

mflipse**NOSPAM**@zonnet.nl

